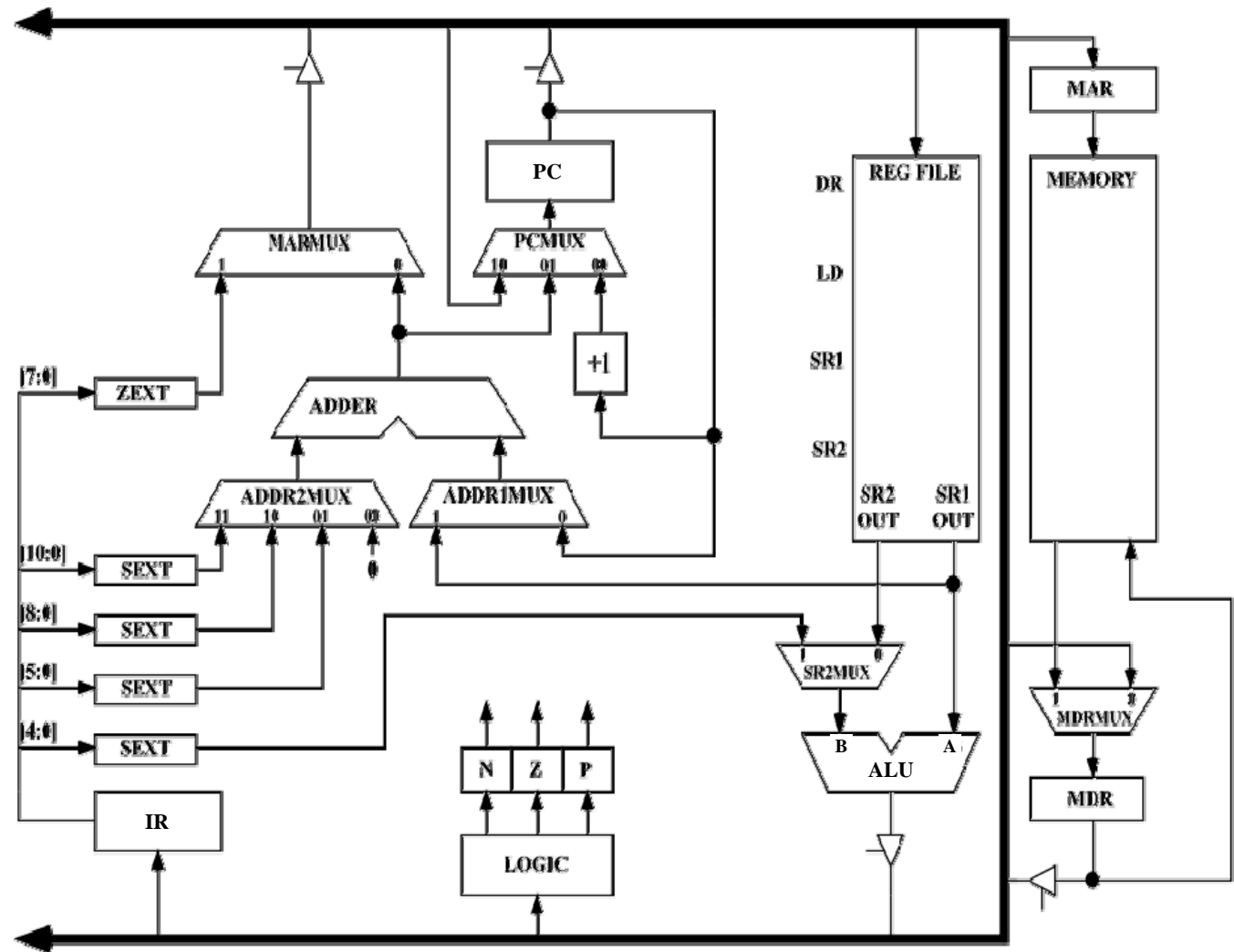


# LC3-1

## The LC-3 A Review



# Introduction


◆ In this class we will:

- Complete the hardware design of the LC-3
- Simulate it
- Run programs on it


# Reference Information

- ◆ You will need the LC-3 Description
- ◆ ECEn 124 / CS 124 Textbook:
  - “Introduction to Computing Systems” (second edition)
  - Yale N. Patt & Sanjay J. Patel
  - McGraw-Hill Higher Education 2004
- ◆ Useful Sections (in order of importance):
  - Appendix A (available on class webpage)
  - Chapter 5
  - Chapter 4
- ◆ Reference material available on the class webpage

# The Von Neumann Model

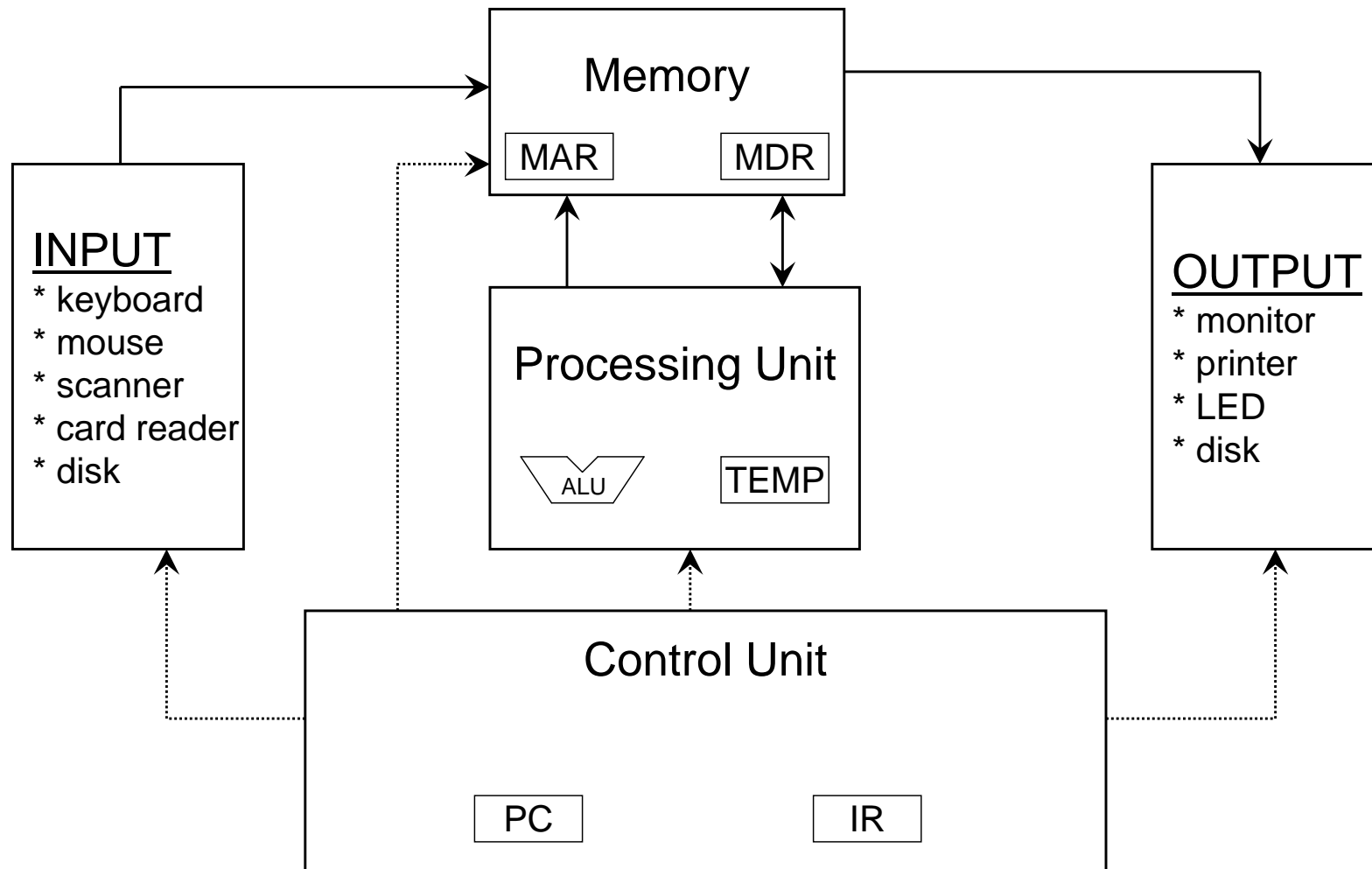


# The Von Neumann Model

 


- ◆ Memory is used to store a sequence of instructions
- ◆ Memory is also used to store data
- ◆ Memory Address Register (MAR) selects which location in memory will be read or written
- ◆ Memory Data Register (MDR) contains the data read or to be written

# The Von Neumann Model

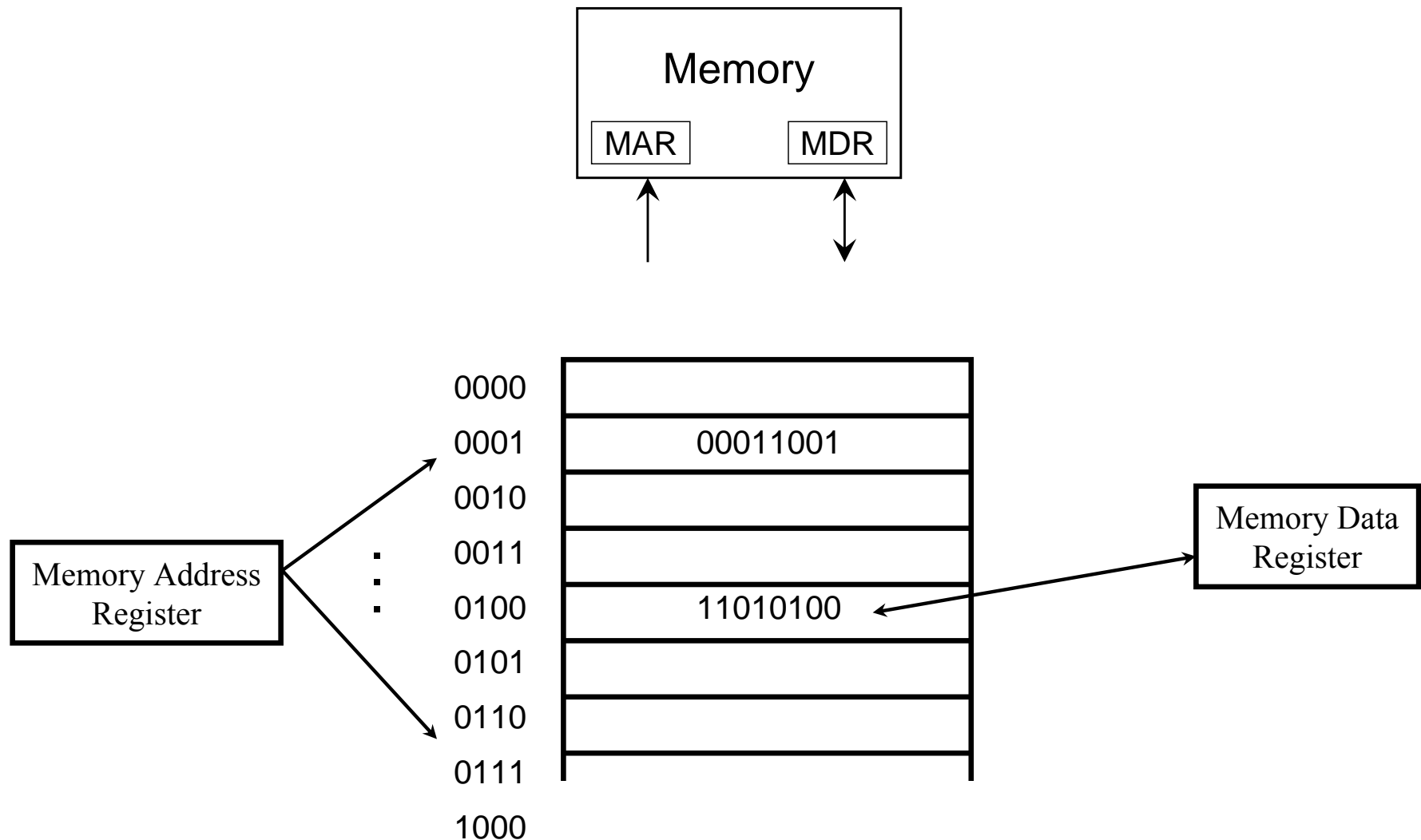

 
# The Von Neumann Model

- ◆ Arithmetic Logic Unit (ALU) does computations and information processing (ADD, AND, NOT, etc.)
- ◆ Registers (TEMP) provide a small amount of high-speed temporary storage



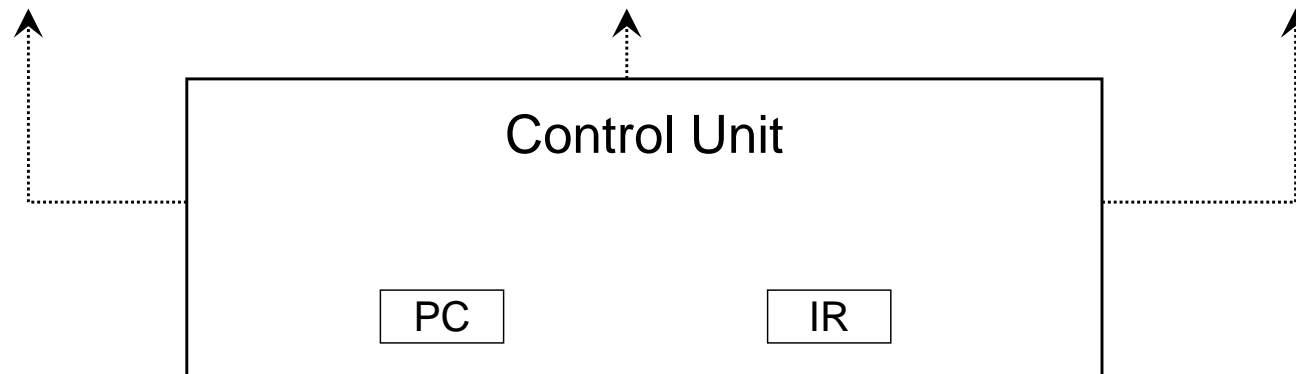
# The Von Neumann Model

- ◆ Control Unit (CU) determines what to do next and controls the rest of the processor
- ◆ Program Counter (PC) contains the address of the next instruction to be executed
- ◆ Instruction Register (IR) contains the current instruction being executed





# The Von Neumann Model

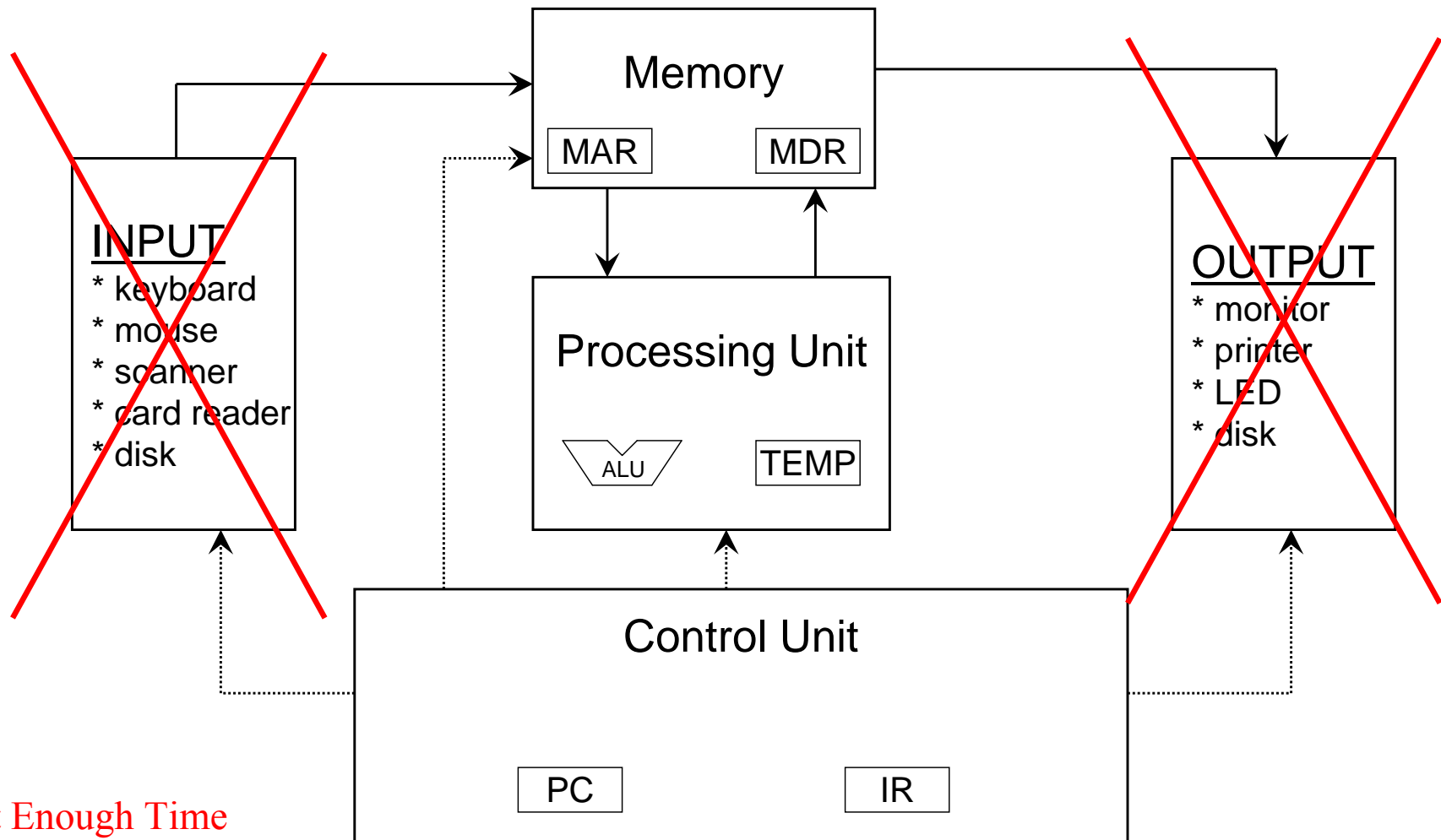


Not Enough Time  
to Study Everything

# The Von Neumann Model

- ◆ Fetch an instruction
- ◆ Execute it
- ◆ Repeat

(Looks a lot like a State Graph)

 

# The Instruction Set Architecture (ISA)

## ◆ ISA for LC-3

- Everything about the computer the software needs to know
  - Memory organization
  - Register set
  - Instruction set
    - Opcodes
    - Data types
    - Addressing modes
- Everything the hardware designer needs to know in order to build a computer
  - Details of how to implement the ISA in hardware are left up to the designer's imagination

# Memory Organization

- ◆ The LC-3 is a 16-bit machine
  - All instructions fit into a 16-bit word
  - Memory is accessed using a 16-bit address word
    - Its address space is  $2^{16}$  locations (65,536 locations)
  - Memory is *word-addressable*
    - Each location is 16-bits wide (2 bytes each)
    - Total memory size is 131,072 bytes
    - The LC-3 is not byte addressable, unlike most machines

# Register Set

- ◆ Memory access is relatively slow
  - It is outside the processing unit
  - It requires completion of an instruction to access (LDR)
- ◆ Registers are *inside* the processing unit
  - They can be accessed *during* an instruction (ADD)
- ◆ Nearly all computers have a *register set*
  - LC-3 has 8 general purpose registers
  - Named R0, R1, ..., R7
  - They are addressed with a 3-bit field in an instruction

# Data Types

- ◆ LC-3 has only one data type
  - 16-bit two's complement integer
- ◆ Other computers have others
  - 32-bit floating point (*float*)
  - 64-bit floating point (*double*)
  - 32-bit signed/unsigned (*int*)
  - 16-bit signed/unsigned (*short*)
  - 8-bit signed/unsigned (*char*)
  - Possibly more...


↑  
These names are  
system dependent

# LC-3 Instructions

ADD	0001	DR	SR1	0	00	SR2
ADD	0001	DR	SR1	1	imm5	
AND	0101	DR	SR1	0	00	SR2
AND	0101	DR	SR1	1	imm5	
NOT	1001	DR	SR	111111		
BR	0000	n	z	p	PCOffset9	
JMP	1100	0	00	BaseR	000000	
JSR	0100	1	PCOffset11			
JSRR	0100	0	00	BaseR	000000	
RET	1100	0	00	111	000000	

LD	0010	DR	PCOffset9										
LDI	1010	DR	PCOffset9										
LDR	0110	DR	BaseR	offset6									
LEA	1110	DR	PCOffset9										
ST	0011	SR	PCOffset9										
STI	1011	SR	PCOffset9										
STR	0111	SR	BaseR	offset6									
TRAP	1111	0000	trapvect8										
RTI	1000	000000000000											
reserved	1101												

# Anatomy of an Instruction

 

This is a 16-bit instruction format.  
The instruction always fills one 16-bit word.



# A Note About Register Notation

- ◆ We will often write things like this:

$$R6 = R5 + R3$$

- ◆ What we mean is:

- The result of adding the *contents of* R5 to the *contents of* R3 is stored into R6

- ◆ What does this mean?

$$R6 = R5 + 7$$

- The result of adding the *contents of* R5 to the integer 7 is stored into R6

# The Instruction Set

- ◆ LC-3 has 16 instructions
- ◆ Three *types* of instructions
  - Operate instructions
    - Operate on data (**ADD R6, R2, R5**)
  - Data movement instructions
    - Memory  $\leftrightarrow$  registers (**LDR R2, R3, #6**)
    - Memory/registers  $\leftrightarrow$  input/output devices
  - Control instructions
    - Change which instruction is executed next (**JMP R3**)

# The Operate Instructions

ADD     

0001	DR	SR1	0	00	SR2
------	----	-----	---	----	-----

 $DR = SR1 + SR2$

ADD     

0001	DR	SR1	1	imm5	
------	----	-----	---	------	--

 $DR = SR1 + \text{SEXT}(\text{imm5})$

AND     

0101	DR	SR1	0	00	SR2
------	----	-----	---	----	-----

 $DR = SR1 \text{ AND } SR2$

AND     

0101	DR	SR1	1	imm5	
------	----	-----	---	------	--

 $DR = SR1 \text{ AND } \text{SEXT}(\text{imm5})$


NOT     

1001	DR	SR	11111		
------	----	----	-------	--	--

 $DR = \text{NOT}(SR)$

# An Operate Instruction

**ADD R6, R2, R5**

 

$$R6 = R2 + R5$$

# The Data Movement Instructions

LD	0010	DR	PCOffset9
----	------	----	-----------

$DR = \text{mem} [ PC + \text{SEXT}(\text{PCOffset9}) ]$

LDI	1010	DR	PCOffset9
-----	------	----	-----------

$DR = \text{mem} [ \text{mem} [ PC + \text{SEXT}(\text{PCOffset9}) ] ]$

LDR	0110	DR	BaseR offset6
-----	------	----	------------------

$DR = \text{mem} [ \text{BaseR} + \text{SEXT}(\text{offset6}) ]$

LEA	1110	DR	PCOffset9
-----	------	----	-----------

$DR = PC + \text{SEXT}(\text{PCOffset9})$

ST	0011	SR	PCOffset9
----	------	----	-----------

$\text{mem} [ PC + \text{SEXT}(\text{PCOffset9}) ] = SR$

STI	1011	SR	PCOffset9
-----	------	----	-----------

$\text{mem} [ \text{mem} [ PC + \text{SEXT}(\text{PCOffset9}) ] ] = SR$

STR	0111	SR	BaseR offset6
-----	------	----	------------------

$\text{mem} [ \text{BaseR} + \text{SEXT}(\text{offset6}) ] = SR$

# An LDR Instruction

**LDR R2, R3, 6**



**Op-Code**  
Tells what the instruction is

**DR**  
Where the value fetched from memory will be placed

**BaseR**  
Where the base address comes from

**Offset6**  
Added to contents of BaseR to generate fetch memory address

**LDR**

**R2**

**R3**

**6**

Offset is sign-extended before being added to base

**EffectiveMemoryAddress  $\leq$  R3 + 6**  
**R2 = MEM[EffectiveMemoryAddress]**

This requires the computation of an effective memory address. It is base + offset. The contents of R3 are the base address and 6 is the offset.

# Control Instructions

BR	0000	n	z	p	PCOffset9
JSR	0100	1			PCOffset11
JSRR	0100	0	00	BaseR	000000
RET	1100	000	111		000000
JMP	1100	000		BaseR	000000
RTI	1000				000000000000
TRAP	1111	0000			trapvect8

PC = PC + SEXT(PCOffset9)  
depending on condition(s)

R7 = PC  
PC = PC + SEXT(PCOffset11)

R7 = PC  
PC = BaseR

PC = R7


PC = BaseR

} Different name,  
same instruction

} Probably won't have time to  
implement these

# A JSRR Instruction

**JSRR R3**

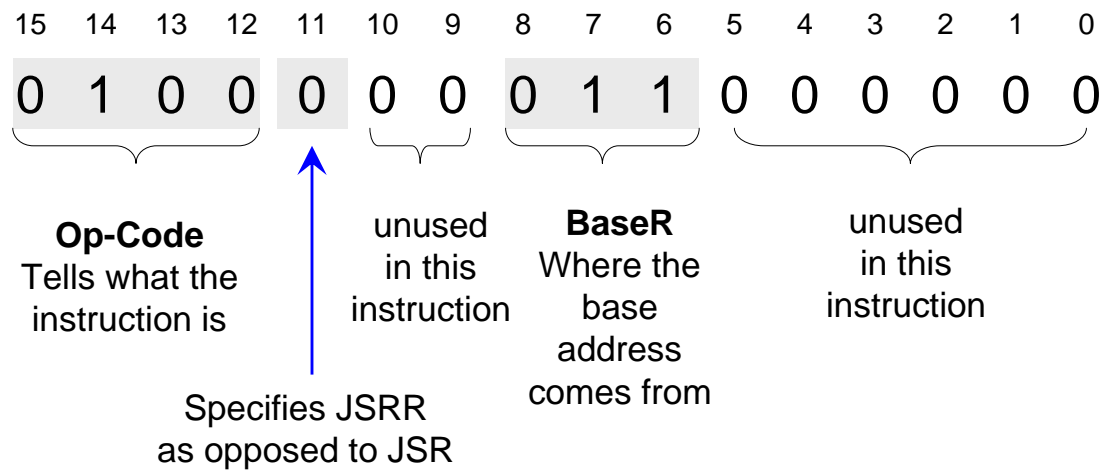

**JSRR**

**R3**

**R7 <= PC**


**PC <= R3**

This is how a subroutine call would be executed.



# A JMP Instruction

**JMP R3**

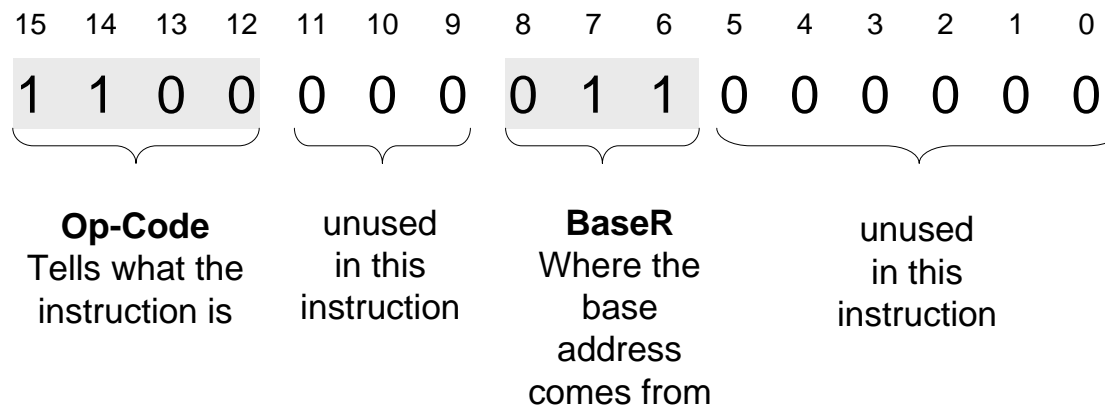

**JMP**

**R3**

**PC <= R3**

This is how a GOTO statement would be executed.

# The LC-3 Architecture

---

## A More Detailed Look

- Common data highway
  - multiple on-ramps and off-ramps
- Most data transfers between units go across the bus
  - Example: PC => MAR
  - Example: MDR => IR


- Can drive 1's and 0's on the bus
- Can disconnect from the bus

[illegible]

# The LC-3 – Instruction Register (IR)

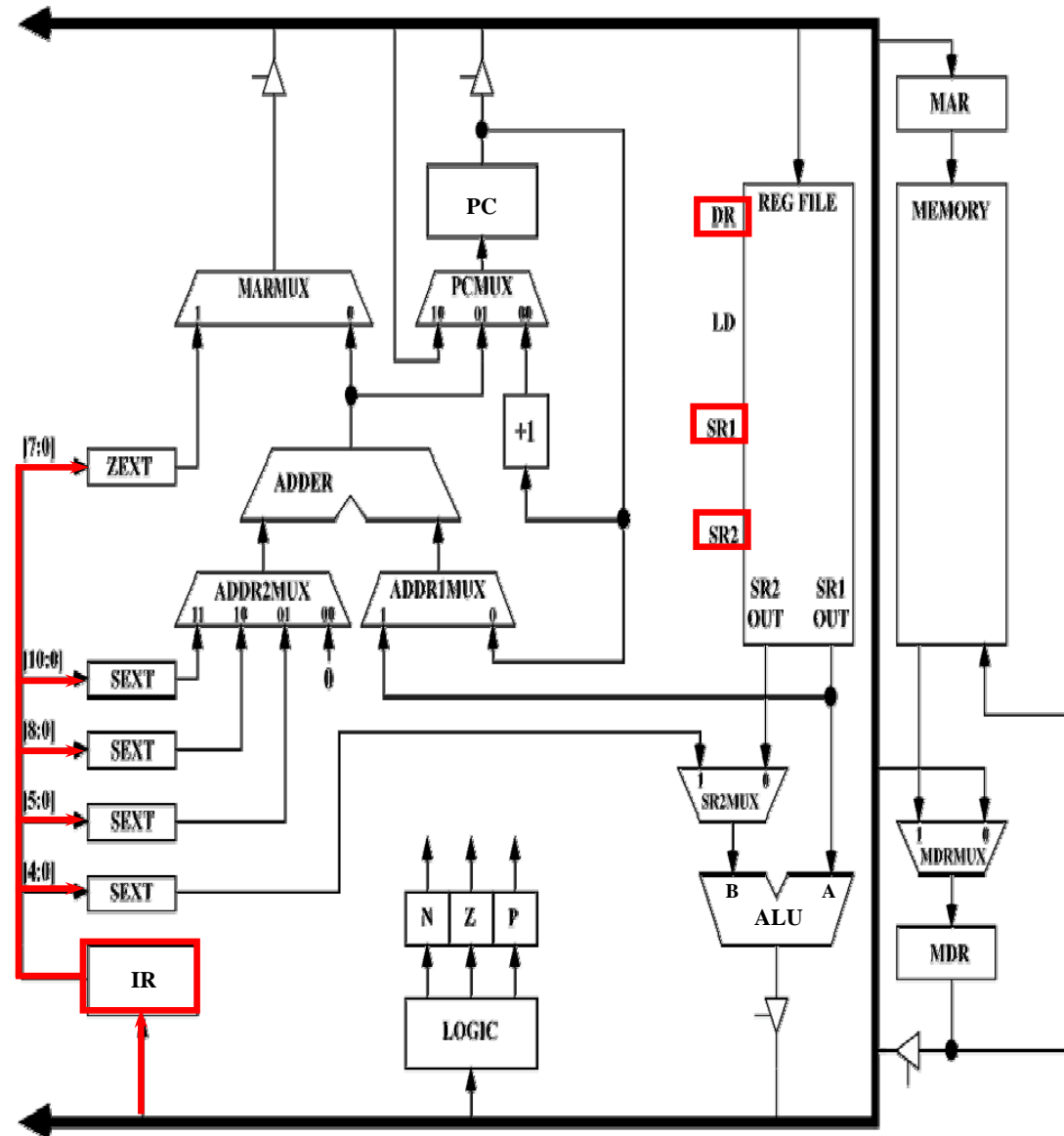
## ◆ The *IR*

- During a fetch the IR is loaded from the bus
- Control unit controls when it should be loaded
- Its fields are pulled apart and fed to many places in the circuit
  - op code
  - source/destination registers
  - immediate data
  - offsets



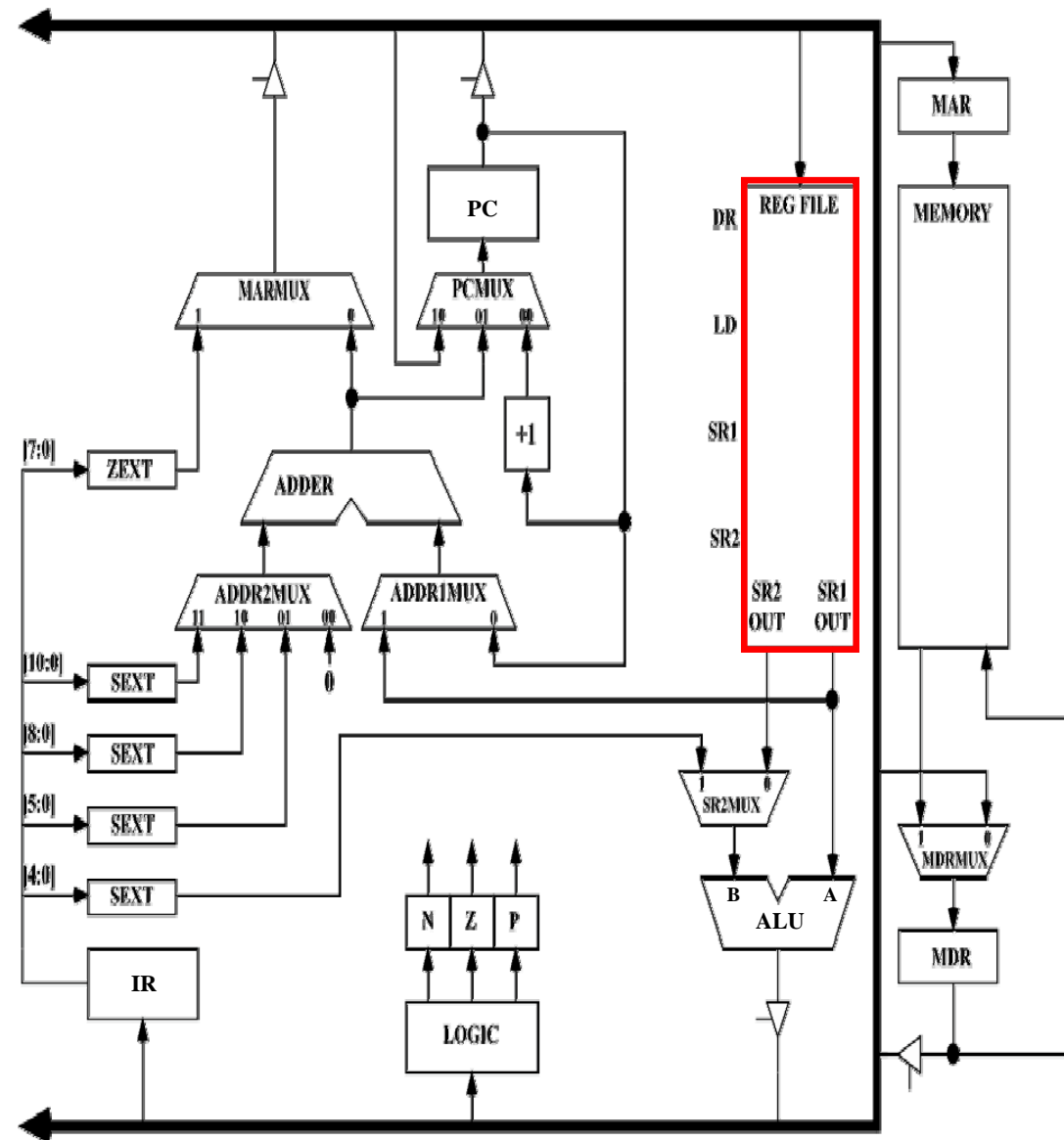
# The LC-3 – Registers

- ◆ The *register file*
  - 8 words of 16-bits each
  - R0-R7
- ◆ Two read address ports
- ◆ One write address port
- ◆ Control unit generates control and address signals
  - To read register file
  - To write back into the register file


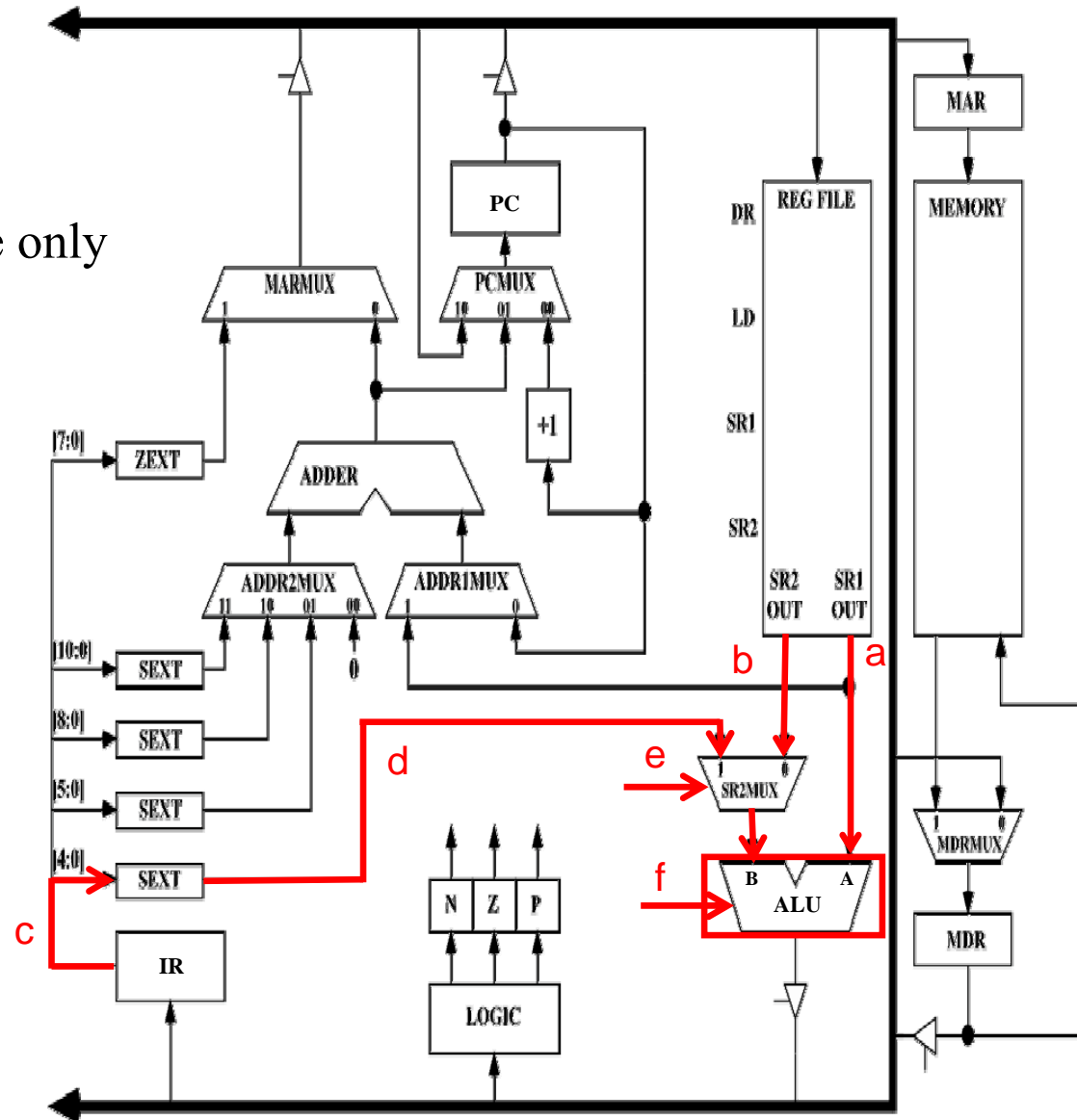
# The LC-3 – ALU

- ◆ The *ALU*
  - Does the arithmetic and logical operations on the data
  - It is *always* working, results are only stored away at the right time
- ◆ One input always comes from register file (a)
- ◆ Second input has two sources
  - register file (b)
  - imm5 from instruction (c)
    - always sign extended (d)
- ◆ Bit 5 of IR selects 2nd input (e)
- ◆ Control unit tells ALU which operation to perform (f)




# The Operate Instructions

ADD	0001	DR	SR1	0	00	SR2	DR = SR1 + SR2
ADD	0001	DR	SR1	1	imm5		DR = SR1 + SEXT(imm5)
AND	0101	DR	SR1	0	00	SR2	DR = SR1 AND SR2
AND	0101	DR	SR1	1	imm5		DR = SR1 AND SEXT(imm5)
NOT	1001	DR	SR	11111			DR = NOT(SR1)
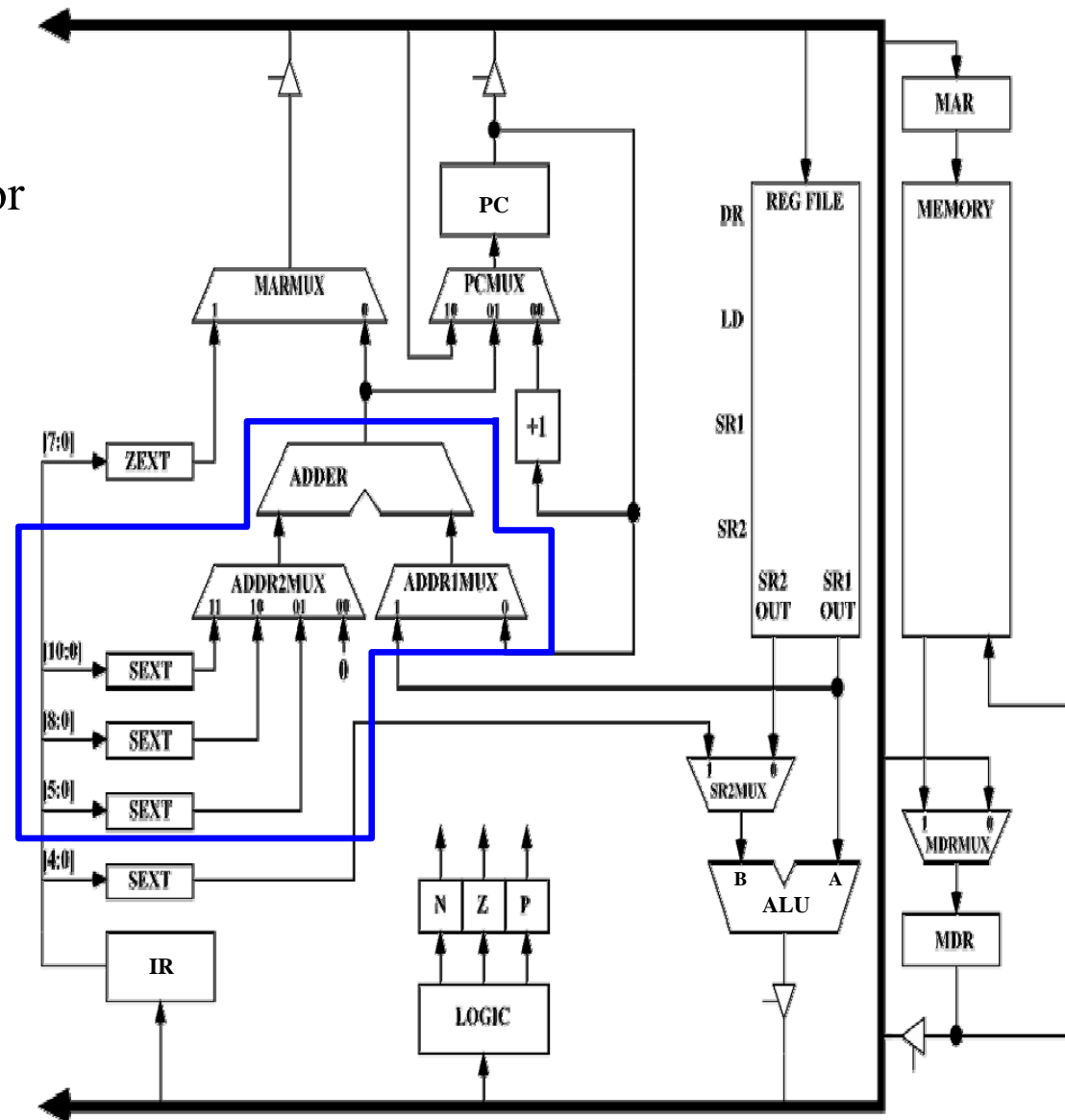
# The LC-3 – Effective Address Block (EAB)

- ◆ The *EAB* (Effective Address Block)
  - Calculates effective addresses for the MAR and the PC





# The LC-3 – EAB

ADD	0001	DR	SR1	0	00	SR2
ADD	0001	DR	SR1	1	imm5	
AND	0101	DR	SR1	0	00	SR2
AND	0101	DR	SR1	1	imm5	
NOT	1001	DR	SR	111111		
BR	0000	n	z	p	PCOffset9	
JMP	1100	0	00	BaseR	000000	
JSR	0100	1	PCOffset11			
JSRR	0100	0	00	BaseR	000000	
RET	1100	0	00	111	000000	

LD	0010	DR	PCoffset9										
LDI	1010	DR	PCoffset9										
LDR	0110	DR	BaseR	offset6									
LEA	1110	DR	PCoffset9										
ST	0011	SR	PCoffset9										
STI	1011	SR	PCoffset9										
STR	0111	SR	BaseR	offset6									
TRAP	1111	0000	trapvect8										
RTI	1000	000000000000											
reserved	1101												

# The LC-3 – EAB

ADD	0001	DR	SR1	0	00	SR2
ADD	0001	DR	SR1	1	imm5	
AND	0101	DR	SR1	0	00	SR2
AND	0101	DR	SR1	1	imm5	
NOT	1001	DR	SR	111111		
BR	0000	n	z	p	PCOffset9	
JMP	1100	0	00	BaseR	000000	
JSR	0100	1	PCOffset11			
JSRR	0100	0	00	BaseR	000000	
RET	1100	0	00	111	000000	

LD	0010	DR	PCOffset9										
LDI	1010	DR	PCOffset9										
LDR	0110	DR	BaseR	offset6									
LEA	1110	DR	PCOffset9										
ST	0011	SR	PCOffset9										
STI	1011	SR	PCOffset9										
STR	0111	SR	BaseR	offset6									
TRAP	1111	0000	trapvect8										
RTI	1000	000000000000											
reserved	1101												

# The LC-3 – EAB

ADD	0001	DR	SR1	0	00	SR2
ADD	0001	DR	SR1	1	imm5	
AND	0101	DR	SR1	0	00	SR2
AND	0101	DR	SR1	1	imm5	
NOT	1001	DR	SR	111111		
BR	0000	n	z	p	PCOffset9	
JMP	1100	0	00	BaseR	000000	
JSR	0100	1	PCOffset11			
JSRR	0100	0	00	BaseR	000000	
RET	1100	0	00	111	000000	

LD	0010	DR	PCOffset9										
LDI	1010	DR	PCOffset9										
LDR	0110	DR	BaseR	offset6									
LEA	1110	DR	PCOffset9										
ST	0011	SR	PCOffset9										
STI	1011	SR	PCOffset9										
STR	0111	SR	BaseR	offset6									
TRAP	1111	0000	trapvect8										
RTI	1000	000000000000											
reserved	1101												


# The LC-3 – EAB

ADD	0001	DR	SR1	0	00	SR2
ADD	0001	DR	SR1	1	imm5	
AND	0101	DR	SR1	0	00	SR2
AND	0101	DR	SR1	1	imm5	
NOT	1001	DR	SR	111111		
BR	0000	n	z	p	PCOffset9	
JMP	1100	0	00	BaseR	000000	
JSR	0100	1	PCOffset11			
JSRR	0100	0	00	BaseR	000000	
RET	1100	0	00	111	000000	

LD	0010	DR	PCOffset9									
LDI	1010	DR	PCOffset9									
LDR	0110	DR	BaseR					offset6				
LEA	1110	DR	PCOffset9									
ST	0011	SR	PCOffset9									
STI	1011	SR	PCOffset9									
STR	0111	SR	BaseR					offset6				
TRAP	1111	0000	trapvect8									
RTI	1000	000000000000										
reserved	1101											
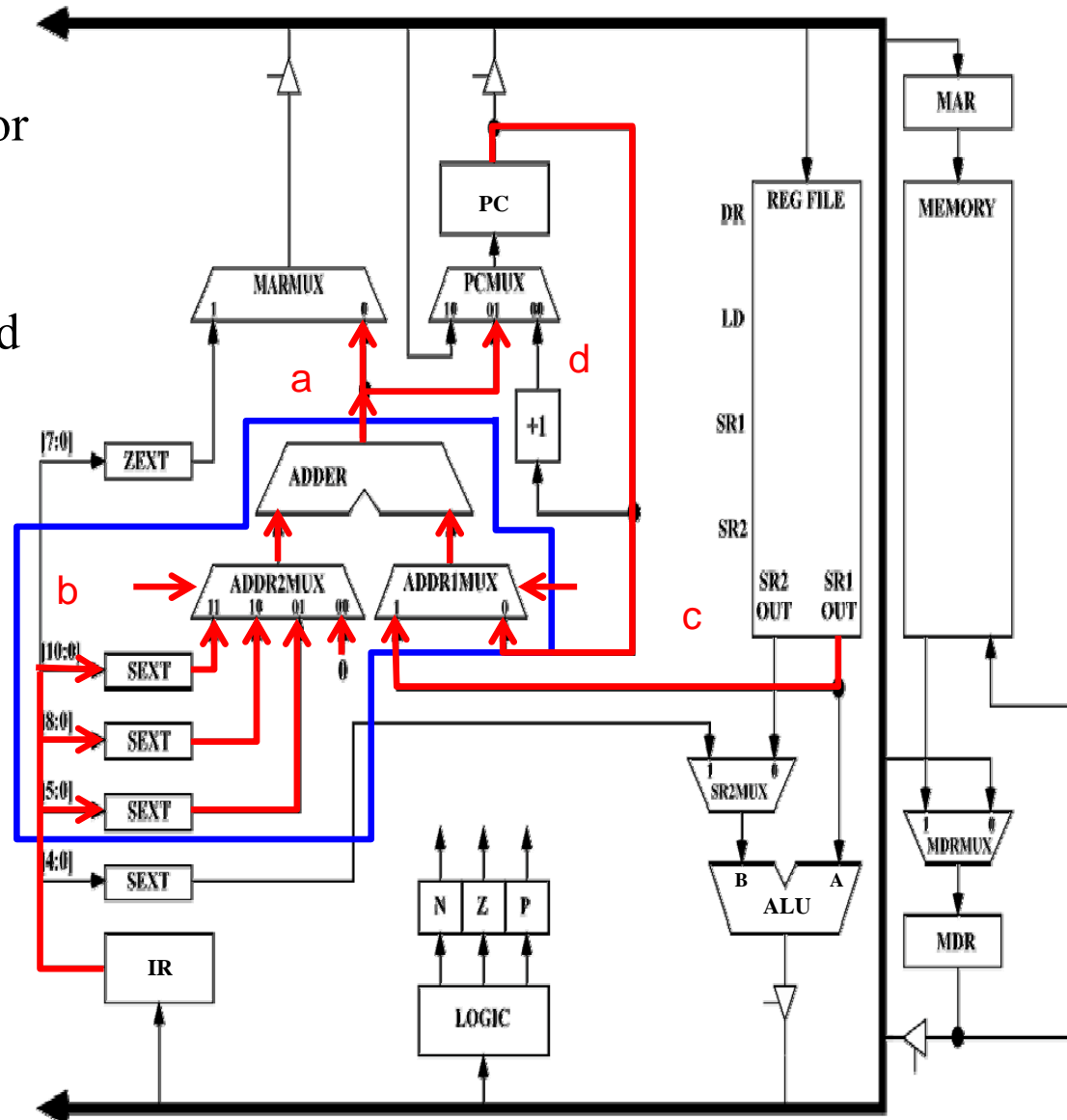
# The LC-3 – EAB

- ◆ The *EAB* (Effective Address Block)
  - Calculates effective addresses for the MAR and the PC
- ◆ It adds two operands that are selected by the control unit (a)
- ◆ One operand is zero or a sign extended field from the IR (10:0, 8:0, or 5:0) (b)
- ◆ The other operand is the current value of the PC or the contents of a register from the register file (c)
- ◆ The sum is passed to both the PCMUX and the MARMUX as an effective address (d)




## ◆ The *Program Counter*

- ## ◆ New PC Computation

- 
- The diagram illustrates the MARS computer architecture, showing the internal components and their interconnections. The architecture is divided into two main sections: the CPU (left) and the Memory (right).
- CPU Section:**
- Instruction Register (IR):** Receives instructions from the Memory Data Register (MDR) and provides a 4-bit address to the ADDR2MUX.
  - Address Register (ADDRMUX):** A 4-to-1 multiplexer that selects between the 4-bit address from the IR and the 4-bit address from the PCMUX. It outputs a 10-bit address to the ADDR2MUX and a 10-bit address to the ADDR1MUX.
  - Address Register (ADDR2MUX):** A 4-to-1 multiplexer that selects between the 10-bit address from the ADDRMUX and the 10-bit address from the PCMUX. It outputs a 10-bit address to the ADDR1MUX.
  - Address Register (ADDR1MUX):** A 4-to-1 multiplexer that selects between the 10-bit address from the ADDR2MUX and the 10-bit address from the PCMUX. It outputs a 10-bit address to the ADDER.
  - Arithmetic Logic Unit (ALU):** Performs arithmetic and logic operations on data from the SR2 and SR1 registers. It outputs a 10-bit result to the MDRMUX.
  - Program Counter (PC):** Holds the current instruction address. It is updated by the PCMUX and outputs a 10-bit address to the ADDRMUX and ADDR2MUX.
  - Program Counter Multiplexer (PCMUX):** A 4-to-1 multiplexer that selects between the 10-bit address from the PC, the 10-bit address from the ADDER, and the 10-bit address from the SR2. It outputs a 10-bit address to the PC.
  - Adder (ADDER):** Adds the 10-bit address from the ADDR1MUX and the 10-bit address from the PCMUX. It outputs a 10-bit address to the PCMUX.
  - Memory Address Register (MAR):** Receives the 10-bit address from the PC and outputs a 10-bit address to the MEMORY.
  - Memory Data Register (MDR):** Receives data from the MEMORY and outputs a 10-bit data to the MDRMUX.
  - Memory Data Register Multiplexer (MDRMUX):** A 4-to-1 multiplexer that selects between the 10-bit data from the MDR and the 10-bit data from the SR2. It outputs a 10-bit data to the MDR.
  - Memory Address Register Multiplexer (MARMUX):** A 4-to-1 multiplexer that selects between the 10-bit address from the PC and the 10-bit address from the ADDRMUX. It outputs a 10-bit address to the MEMORY.
  - Register File (REG FILE):** Contains two registers, SR1 and SR2. It receives data from the MDRMUX and outputs 10-bit data to the PCMUX and the ALU.
  - Logic (LOGIC):** Receives the 10-bit data from the ALU and outputs three status flags: N (Negative), Z (Zero), and P (Positive).
- External Components:**
- PC (Program Counter):** A 10-bit register that holds the current instruction address.
  - PCMUX (Program Counter Multiplexer):** A 4-to-1 multiplexer that selects between the 10-bit address from the PC, the 10-bit address from the ADDER, and the 10-bit address from the SR2.
  - ADDER (Adder):** A 10-bit adder that adds the 10-bit address from the ADDR1MUX and the 10-bit address from the PCMUX.
  - ADDRMUX (Address Register Multiplexer):** A 4-to-1 multiplexer that selects between the 10-bit address from the IR and the 10-bit address from the PCMUX.
  - ADDR2MUX (Address Register Multiplexer):** A 4-to-1 multiplexer that selects between the 10-bit address from the ADDRMUX and the 10-bit address from the PCMUX.
  - ADDR1MUX (Address Register Multiplexer):** A 4-to-1 multiplexer that selects between the 10-bit address from the ADDR2MUX and the 10-bit address from the PCMUX.
  - SR2MUX (Status Register Multiplexer):** A 4-to-1 multiplexer that selects between the 10-bit data from the MDRMUX and the 10-bit data from the SR2.
  - MDRMUX (Memory Data Register Multiplexer):** A 4-to-1 multiplexer that selects between the 10-bit data from the MDR and the 10-bit data from the SR2.
  - MARMUX (Memory Address Register Multiplexer):** A 4-to-1 multiplexer that selects between the 10-bit address from the PC and the 10-bit address from the ADDRMUX.
  - REG FILE (Register File):** A component that contains two registers, SR1 and SR2, and outputs 10-bit data to the PCMUX and the ALU.
  - LOGIC (Logic):** A component that receives the 10-bit data from the ALU and outputs three status flags: N (Negative), Z (Zero), and P (Positive).
- The diagram is labeled with 'a', 'b', and 'c' to indicate specific components or data paths.
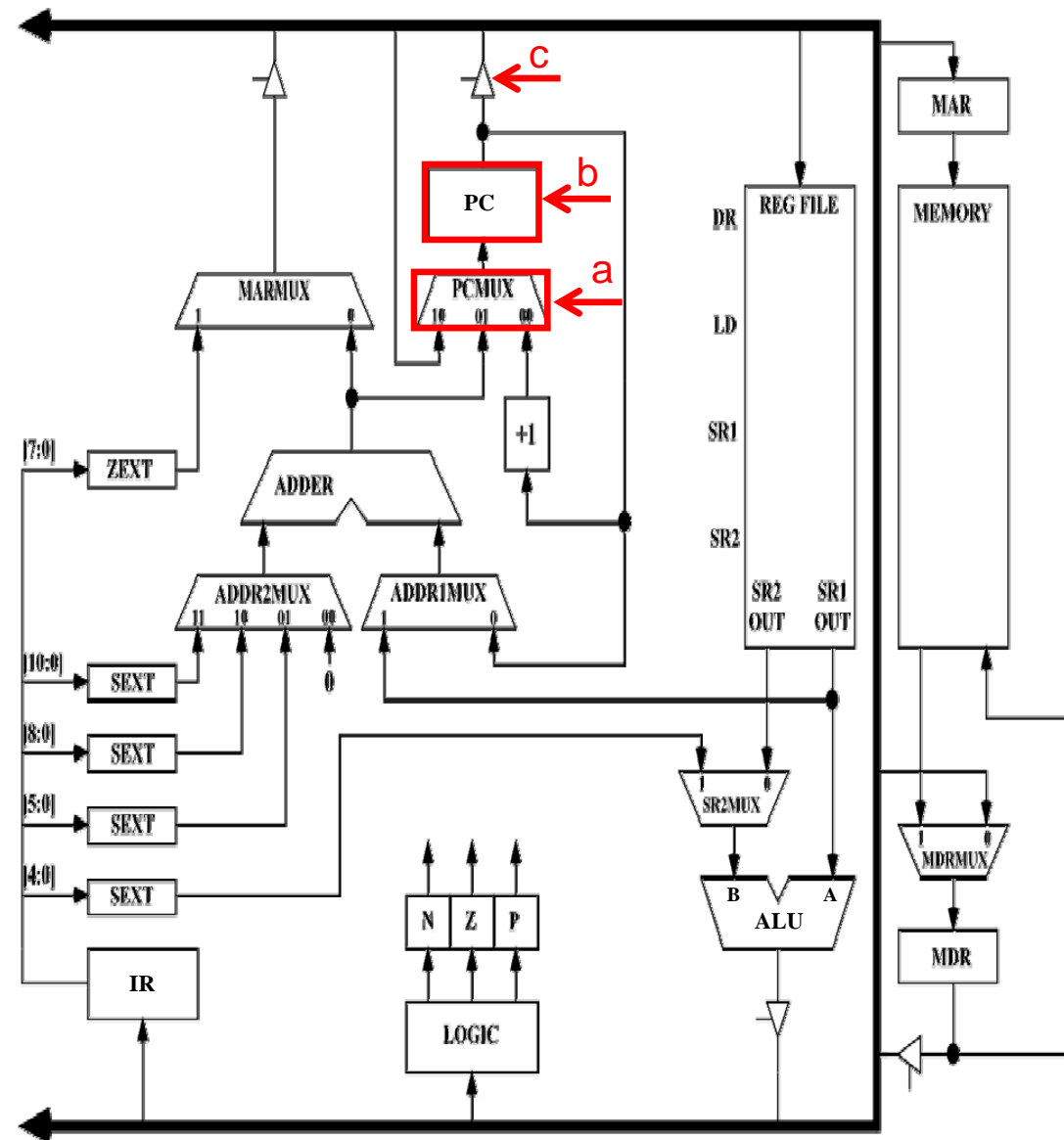
# The LC-3 – PC and PCMUX

- ◆ Control unit controls loading of PC
  - Selects which value it should load (a)
  - Tells *when* PC should load a new value (b)
- ◆ Control unit tells PC when to drive onto global bus (c)



# The LC-3 – MARMUX


## ◆ The *MARMUX*

- Selects what address is driven onto global bus for loading into the MAR
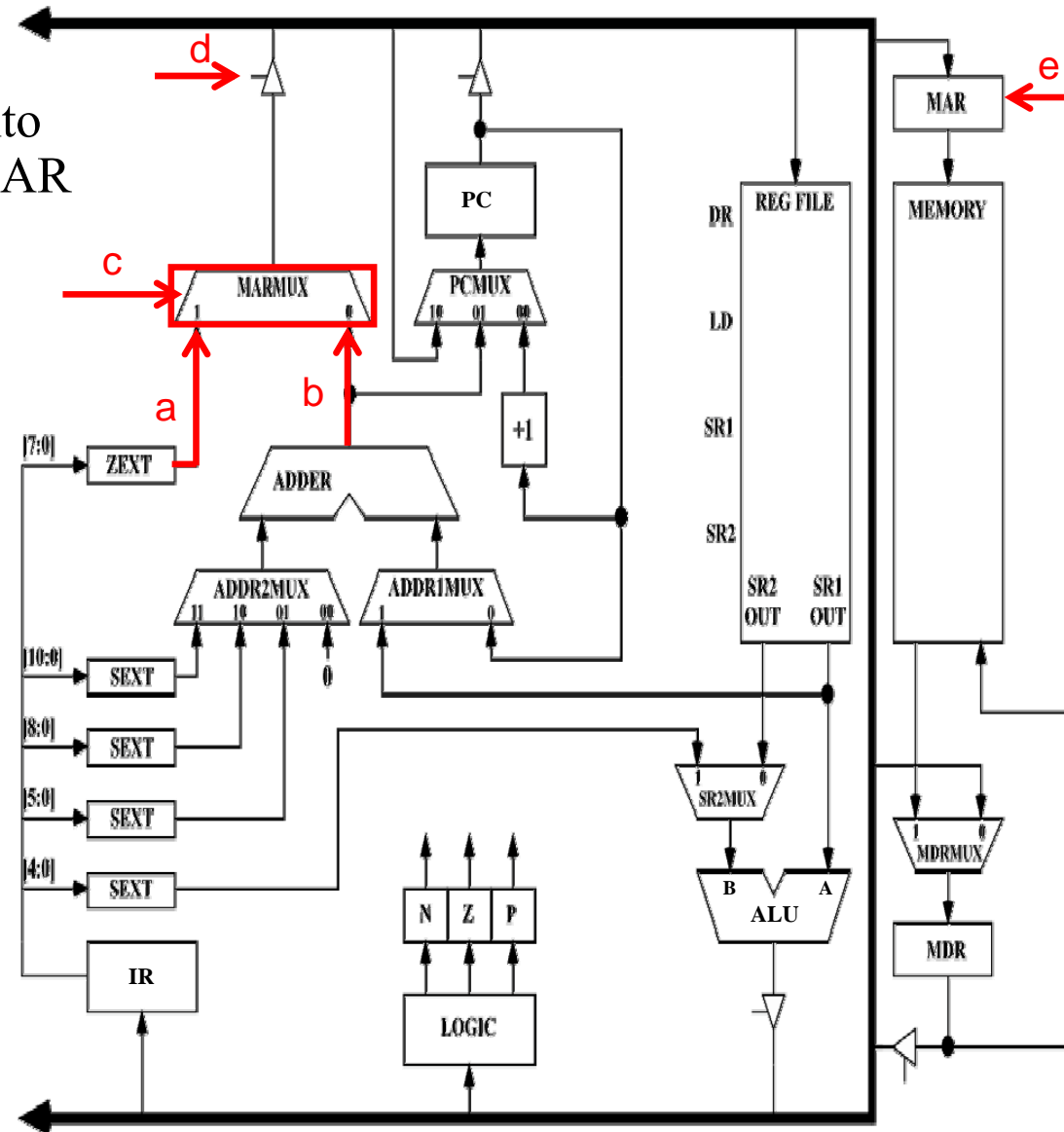
## ◆ *MARMUX* Sources

- Can be IR<sub>7:0</sub> zero extended (a)
  - For TRAP instructions
- Can be output of EAB (b)
  - For load instructions


- ◆ Control unit selects source (c), controls driving it out onto global bus (d), and when MAR is loaded (e)





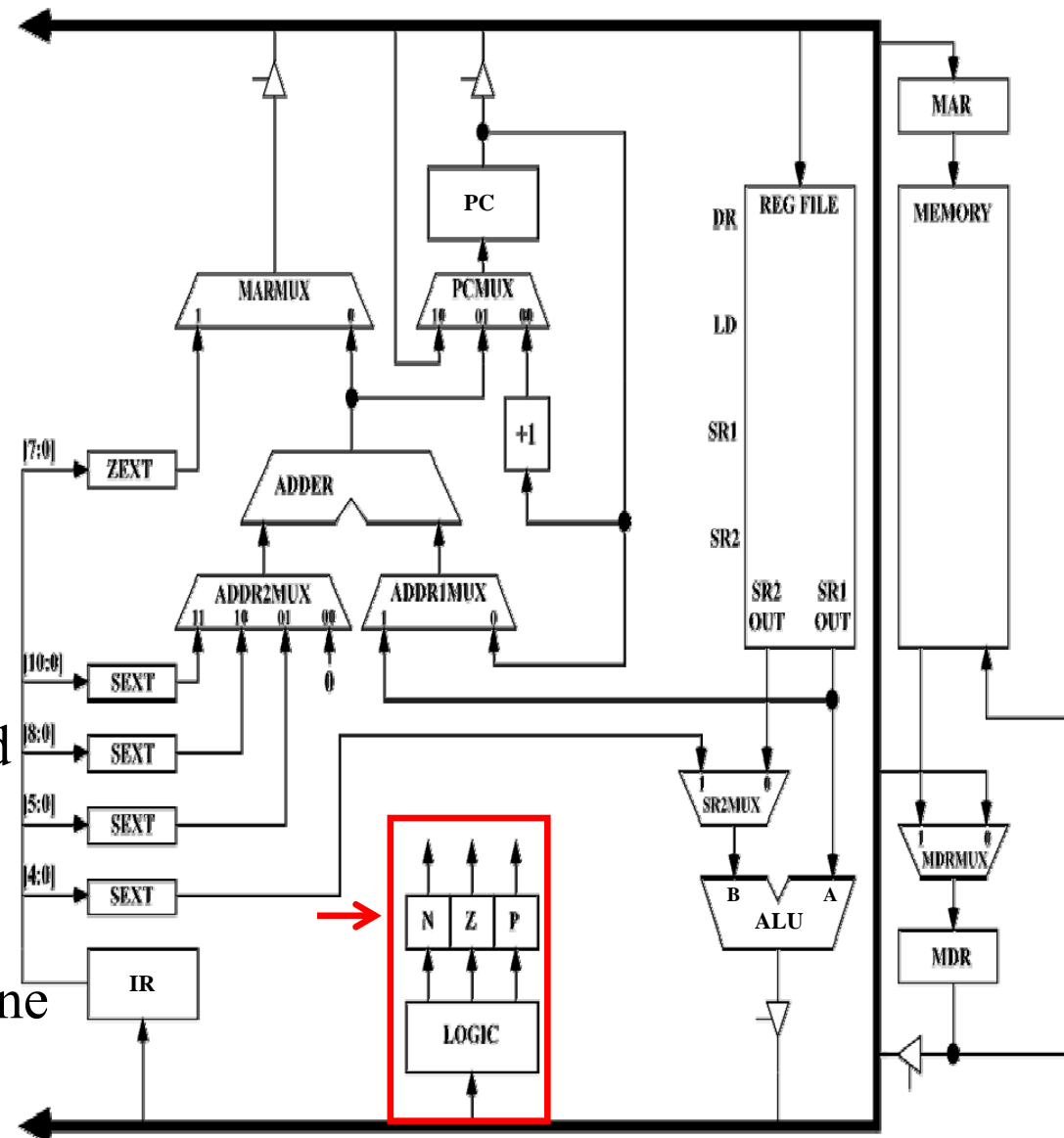
# The LC-3 – N, Z, P Condition Codes

- ◆ The condition code registers
  - 1-bit each
- ◆ Logic block monitors global bus values
  - It continuously outputs whether bus value is negative, zero, or positive
- ◆ Control unit controls when N, Z, and P registers are actually loaded
  - They are loaded on arithmetic and load instructions
- ◆ Control unit uses them to determine whether or not to branch on BR


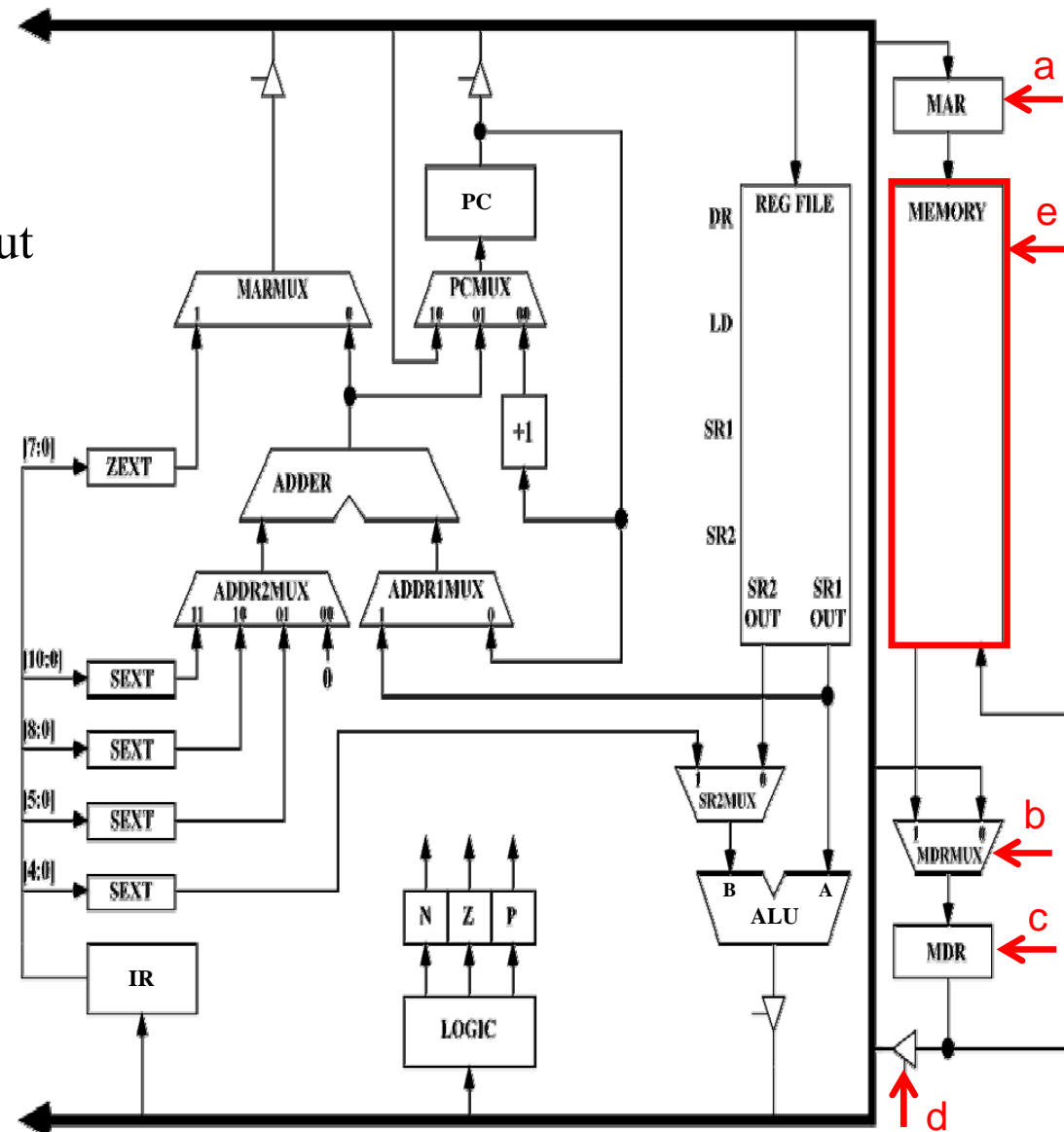
# The Memory

- ◆ On a read:
  - Address comes from MAR
  - Data is put into MDR and then out onto the bus
- ◆ On a write:
  - Address comes from MAR
  - Data to be written comes from MDR
- ◆ Control unit tells memory when to load MAR (a), what value to pass through the MDRMUX (b), when to load MDR (c), when to drive the value in the MDR onto global bus (d), and when to write to memory (e).




# Data Flow

---

## Tracing Data And The Execution of Instructions Through LC-3

 
# The Von Neumann Model

- ◆ Fetch an instruction
- ◆ Execute it
- ◆ Repeat


 
# Example Instruction


- ◆ **ADD R5, R2, R6**
- ◆ Operands must already be in registers



$$R5 = R2 + R6$$
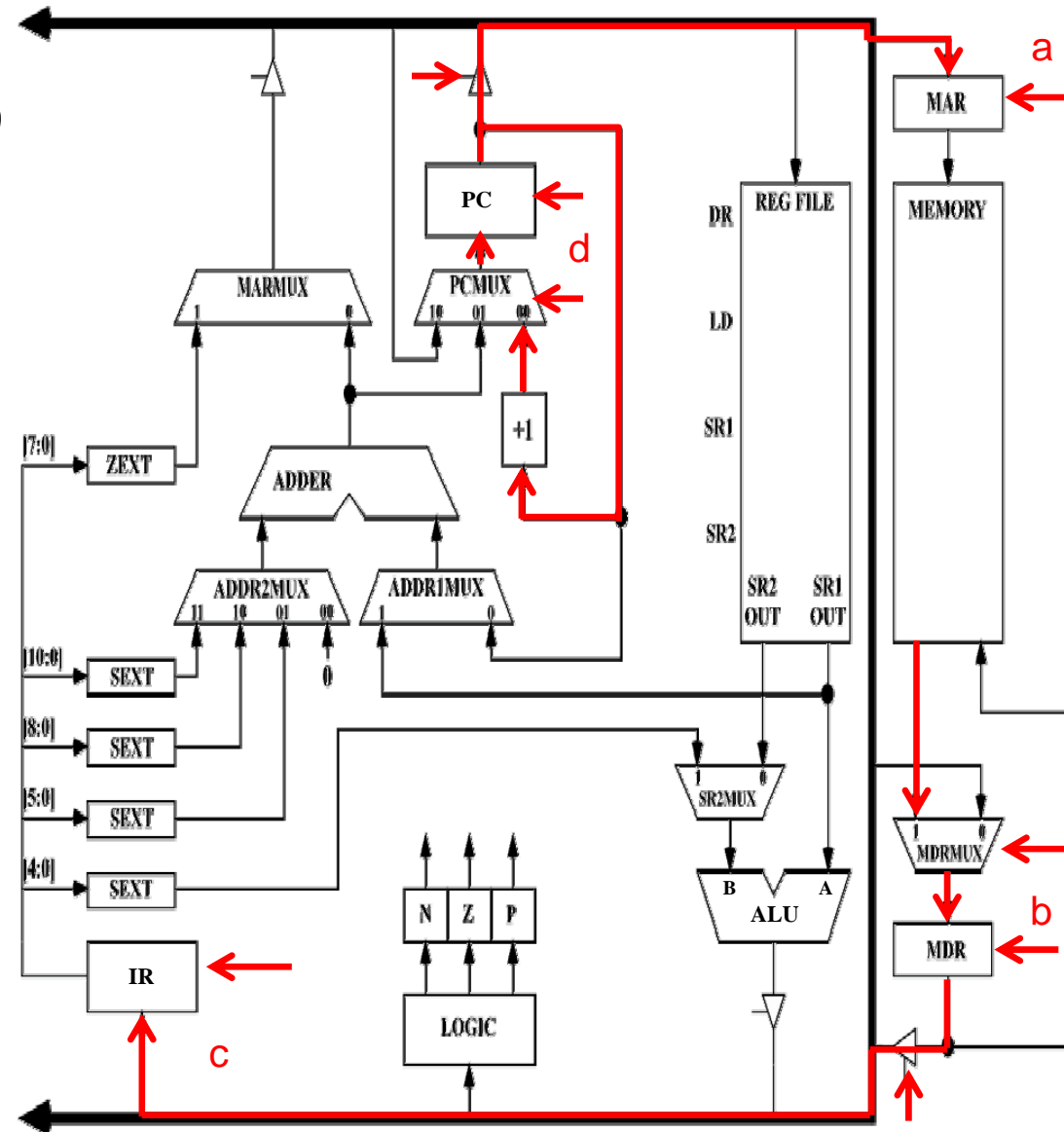
# Instruction Fetch

- ◆ Copy the PC into the MAR (a)
- ◆ Load Memory Output into MDR (b)
- ◆ Load Output of MDR into IR (c)
- ◆ Increment PC (d)




0001	101	010	0	00	110
ADD	DR	SR1			SR2

-
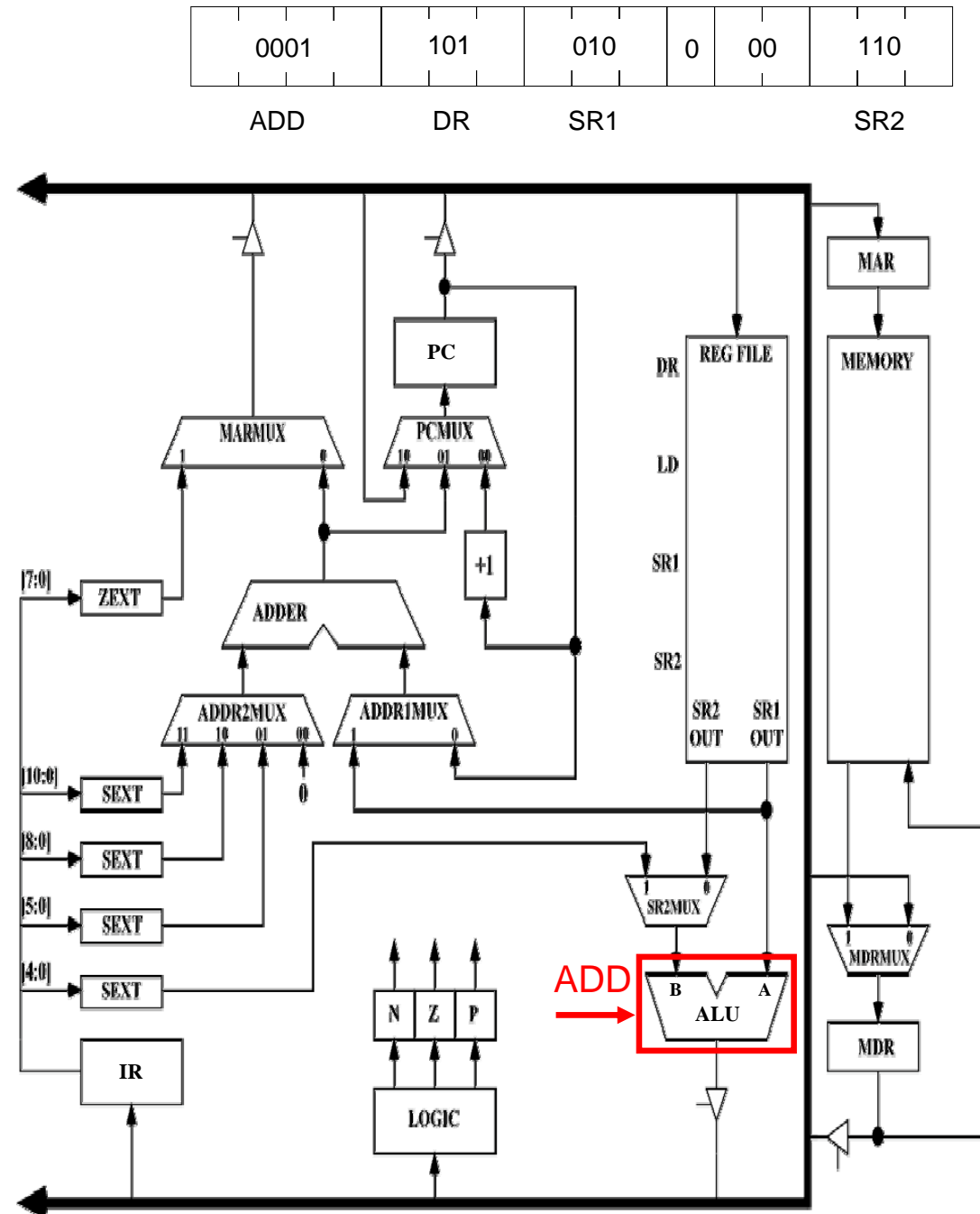
# Execute


- ◆ The ALU does the addition
  - Control unit tells it which operation to do (ADD)




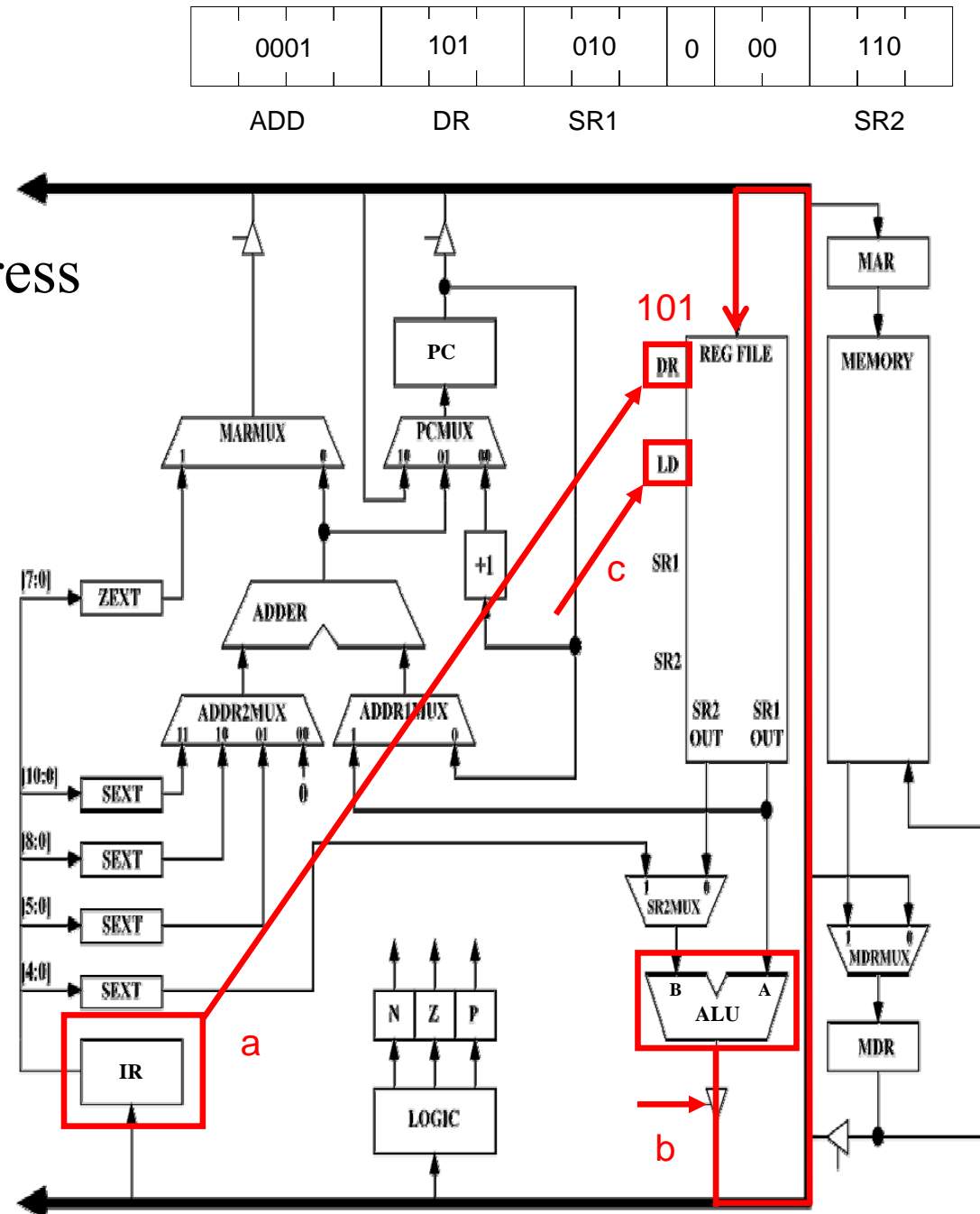
# Store Result


- ◆ Send DR field from IR as address to the register file (a)
- ◆ Enable ALU output to pass onto the bus (b)
- ◆ Store ALU output into DR by enabling register file load (c)



# Another Example Instruction

◆ **STR R2, R3, 9**

◆ Numbers must already be in registers

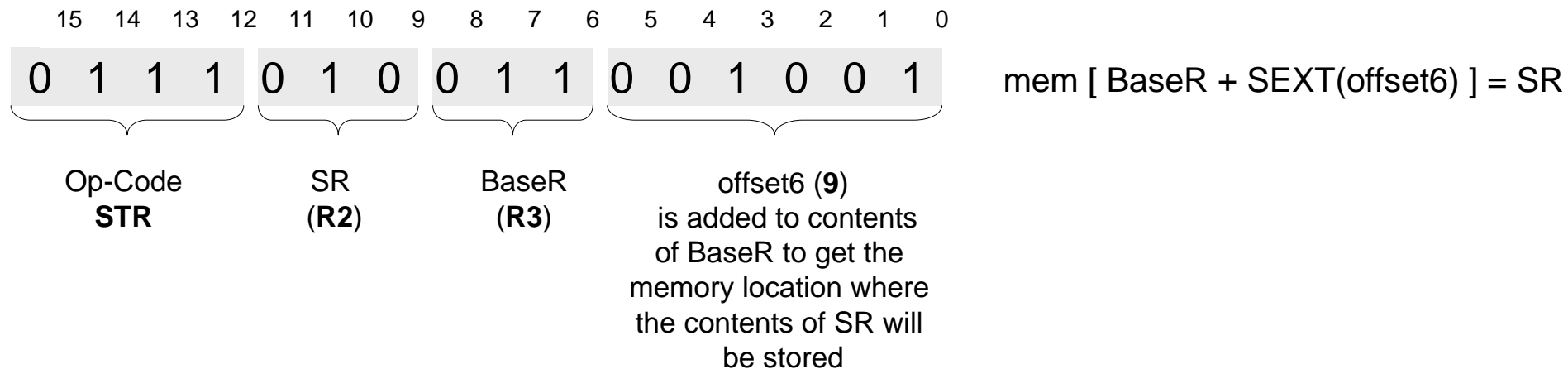


**EffectiveMemoryAddress  $\leq$  R3 + 9**  
**mem[EffectiveMemoryAddress] = R2**

# STR – Instruction Fetch

Same as ADD Instruction
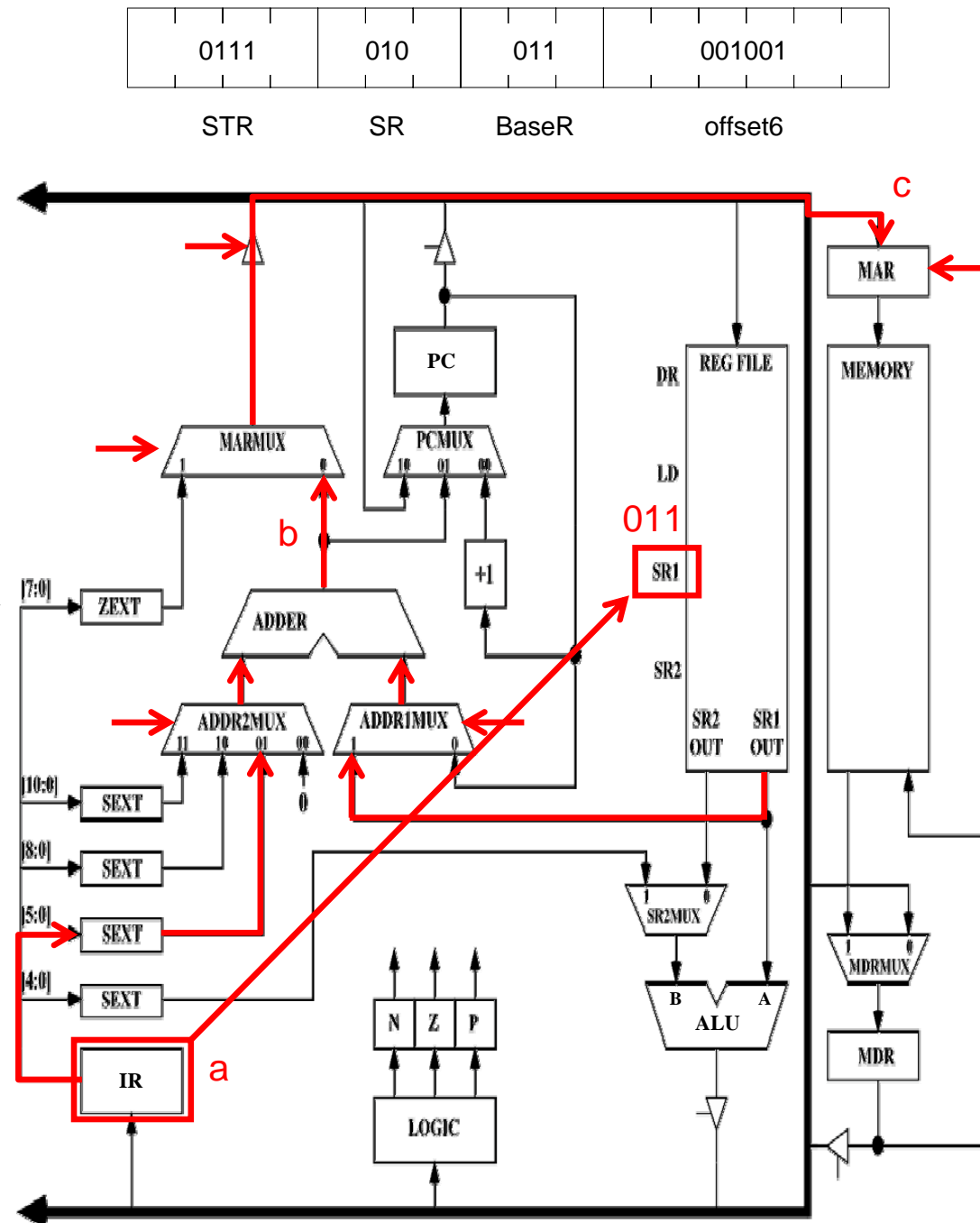
# STR


- ◆ Send BaseR field from IR as address to the register file (a)
- ◆ Add the contents of BaseR to the sign extended offset6 from the IR to form the destination memory address for the STR (b)
- ◆ Store the generated address into the MAR (c)



# STR

0111	010	011	001001
STR	SR	BaseR	index6

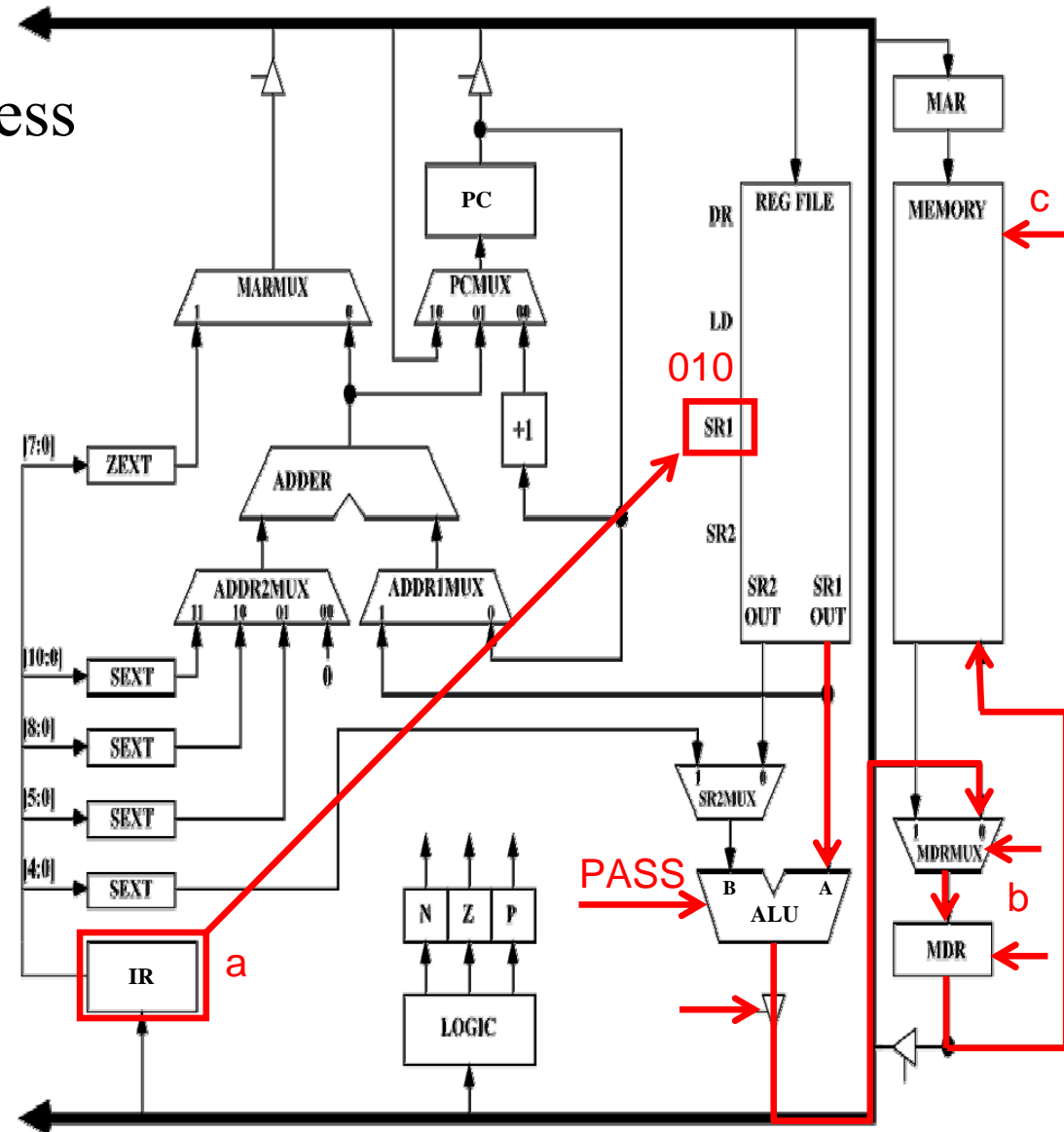
- ◆ Send SR field from IR as address to the register file (a)
- ◆ Store the contents of SR to the MDR (b)
- ◆ Perform the memory write (c)



# Another Example Instruction

## ◆ **BRnz LABEL**
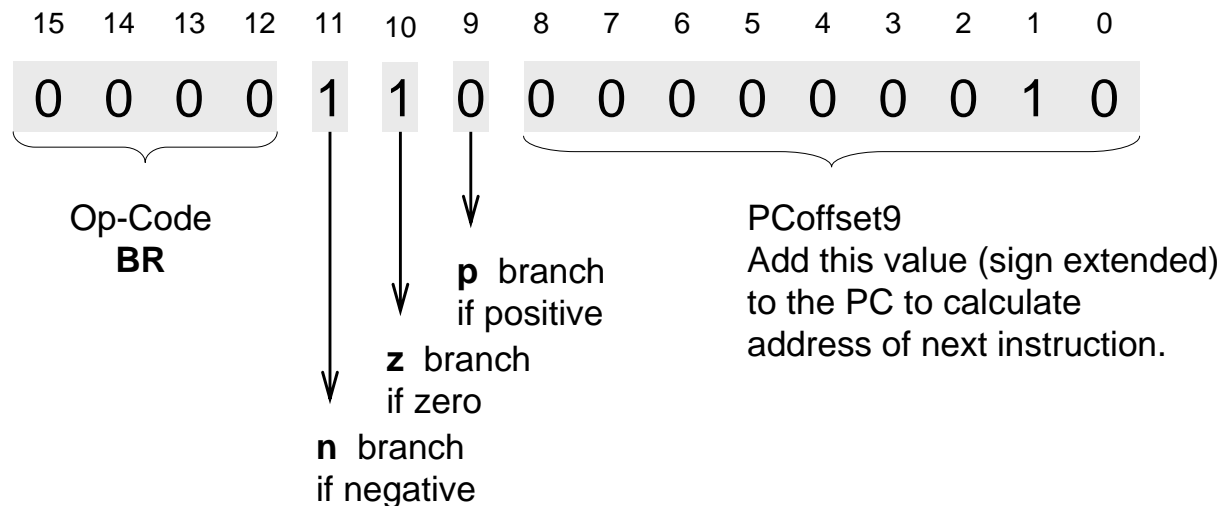
## ◆ Condition Codes loaded by previous instruction



if (n AND N) OR (z AND Z) OR (p AND P)


PC = PC + PCOffset9

# What are Condition Codes ?

- ◆ LC-3 contains 3 special registers
  - 1-bit wide each
  - Named N, Z, P (negative, zero, positive)
- ◆ For most instructions, when a register is written with a new value then N, Z, and P are updated to reflect the value written
- ◆ Only specific instructions modify the condition codes
  - See back cover or appendix of ECEn/CS 124 book to be sure

# All Instructions

ADD	0001	DR	SR1	0	00	SR2
ADD	0001	DR	SR1	1	imm5	
AND	0101	DR	SR1	0	00	SR2
AND	0101	DR	SR1	1	imm5	
NOT	1001	DR	SR	111111		
BR	0000	n	z	p	PCOffset9	
JMP	1100	0	00	BaseR	000000	
JSR	0100	1	PCOffset11			
JSRR	0100	0	00	BaseR	000000	
RET	1100	0	00	111	000000	
LD	0010	DR	PCOffset9			
LDI	1010	DR	PCOffset9			
LDR	0110	DR	BaseR	offset6		
LEA	1110	DR	PCOffset9			
ST	0011	SR	PCOffset9			
STI	1011	SR	PCOffset9			
STR	0111	SR	BaseR	offset6		
TRAP	1111	0000	trapvect8			
RTI	1000	000000000000				
reserved	1101					

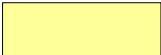
 ⇒ Instruction sets condition codes N Z P




# An if Statement Using BR

Address


x3000

 


x3001

 


x3002

 


x3003

 

x3004

 

x3005

 


if (a > 0)  
 a = 15 ;  
 a = a + 1 ;



# BRnz Instruction Fetch

Same as ADD Instruction

# BRnz – Execution

 

- ◆ Compare n and z in IR to N and Z registers
- ◆ Generate branch address  $PC + \text{SEXT}(\text{PCOffset9})$  (a)
- ◆ Pass new address through the PCMUX (b)
- ◆ Load branch address into PC iff the condition codes match (c)

